

Impedance Spectroscopy


Using the Matlab program

ZfitGUI



Theory and other things may be found in the Macdonal book and here :

<https://sites.google.com/site/jeanlucdellis>

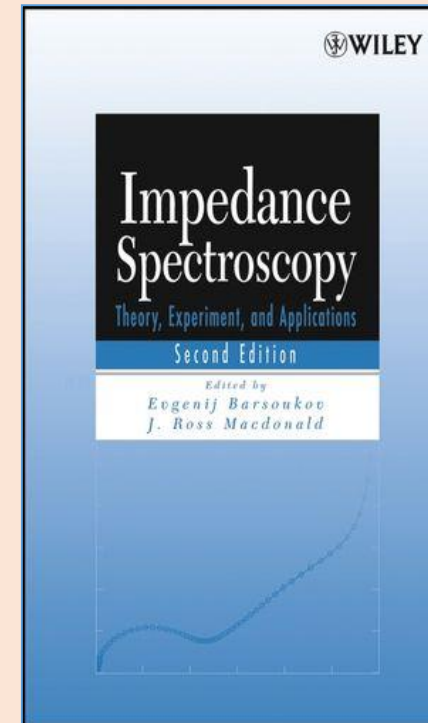(in the « programmes Matlab » and in the « Spectroscopie d'Impédance » repertories)




Download the Matlab program ZfitGUI

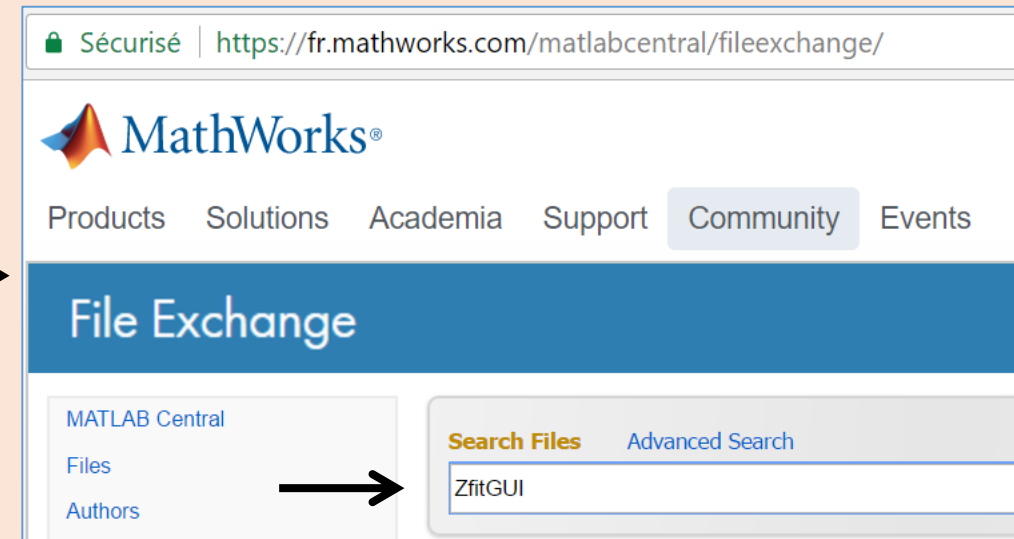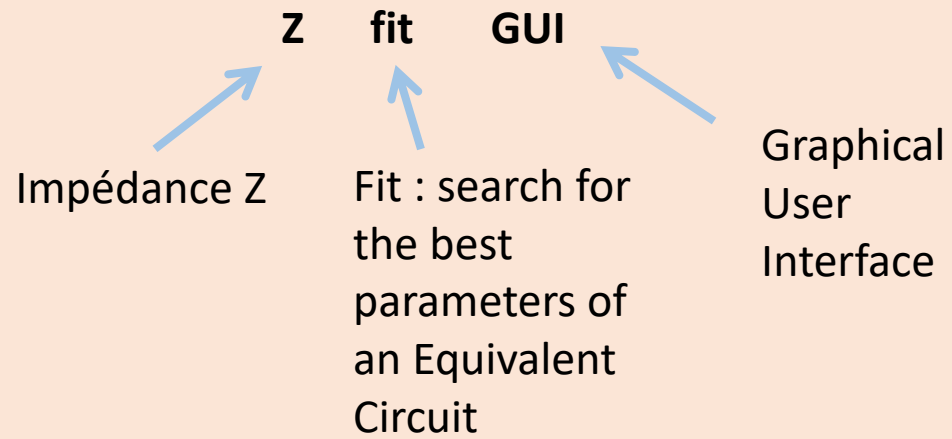


Preamble

Impedance is a complex number $Z = Z_r + jZ_i$ which is frequency dependent as are the related immittances like for instance, the complex capacitance : $C = \frac{1}{jZ\omega}$. The curve $Z_i = f(Z_r)$ is called spectrum as well as $C_i = f(C_r)$. To model these data, one may use equivalent circuit (EC). The spectra have usually one or more semi-circle loops whose analysis allows to separate intrinsic phenomena of those arising from the electrodes, the wires or even the apparatus effects.

- If a semi-circle is found in the Z-representation, one may use the parallel model $p(R1,C1)$. It means that when the EC is submitted to a voltage, the current comes from 2 additive contributions. One is dissipative $i_1 = \frac{u}{R}$ when the other is conservative $i_2 = C \frac{du}{dt}$. If the semi-circle was shifted along the real Z axis, just add a resistor in series to fit the spectrum. In the same vein, note that the series EC $s(p(R1,C1), p(R1,C1))$ will give 2 successive semi-circles, less or more overlapped.

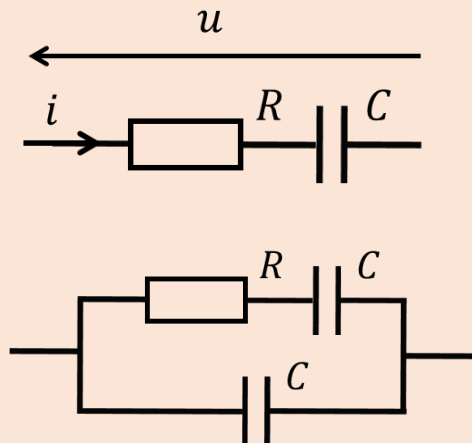

- If the semi-circle was found in the C-representation, the right EC is the serial Debye model $s(R1,C1)$ with only one current usually attributed to the material polarization and which equilibrium is delayed by the resistor. If the semi-circle was shifted along the real C axis, just add a capacitor in parallel to fit the data. Here also, we may find 2 successive semi-circles but the model would be : $p(s(R1,C1), s(R1,C1))$.

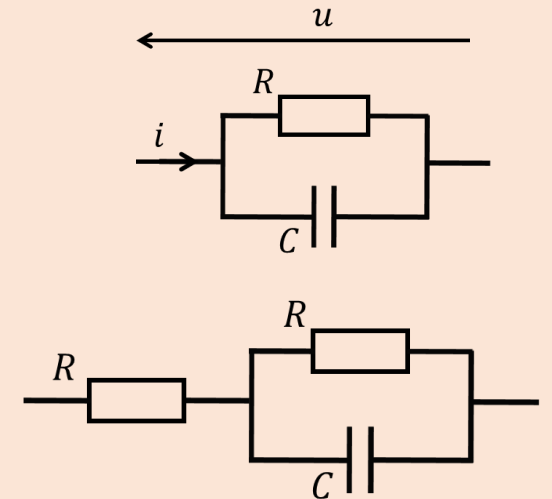


Download simulations and experimental data

In Internet, search for the google web site « jeanlucdellis », navigate to the « programmes Matlab » repertory to download the files to process as trainings.


<https://sites.google.com/site/jeanlucdellis/>

programmes **Matlab**

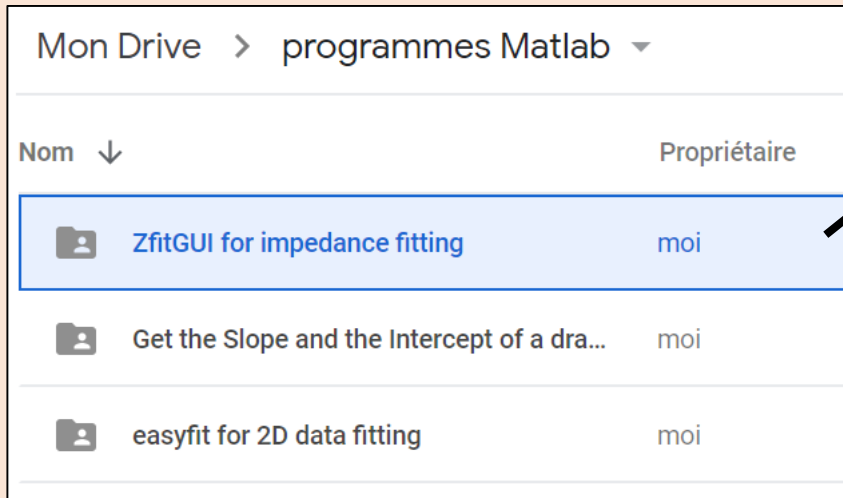

- C2Loops.mat
- circle123.mat
- circuit1.mat
- circuit2.mat
- circuit3.mat
- Legreen.mat
- Maruse.mat
- Panata.mat
- Z2Loops.mat

Download

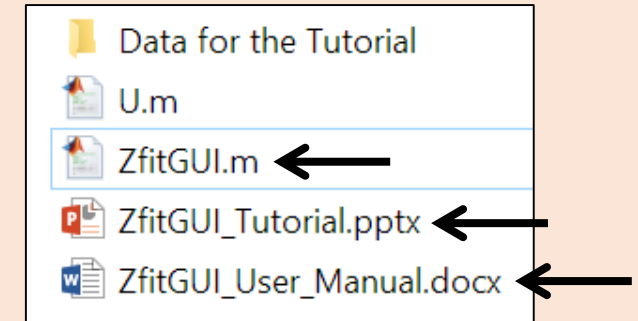


Get the function ZfitGUI, the Tutorial and the User Manual


the Matlab program ZfitGUI adds UIMENUS to a figure

Type ZfitGUI without inputs :

```
Command Window  
fx >> ZfitGUI
```

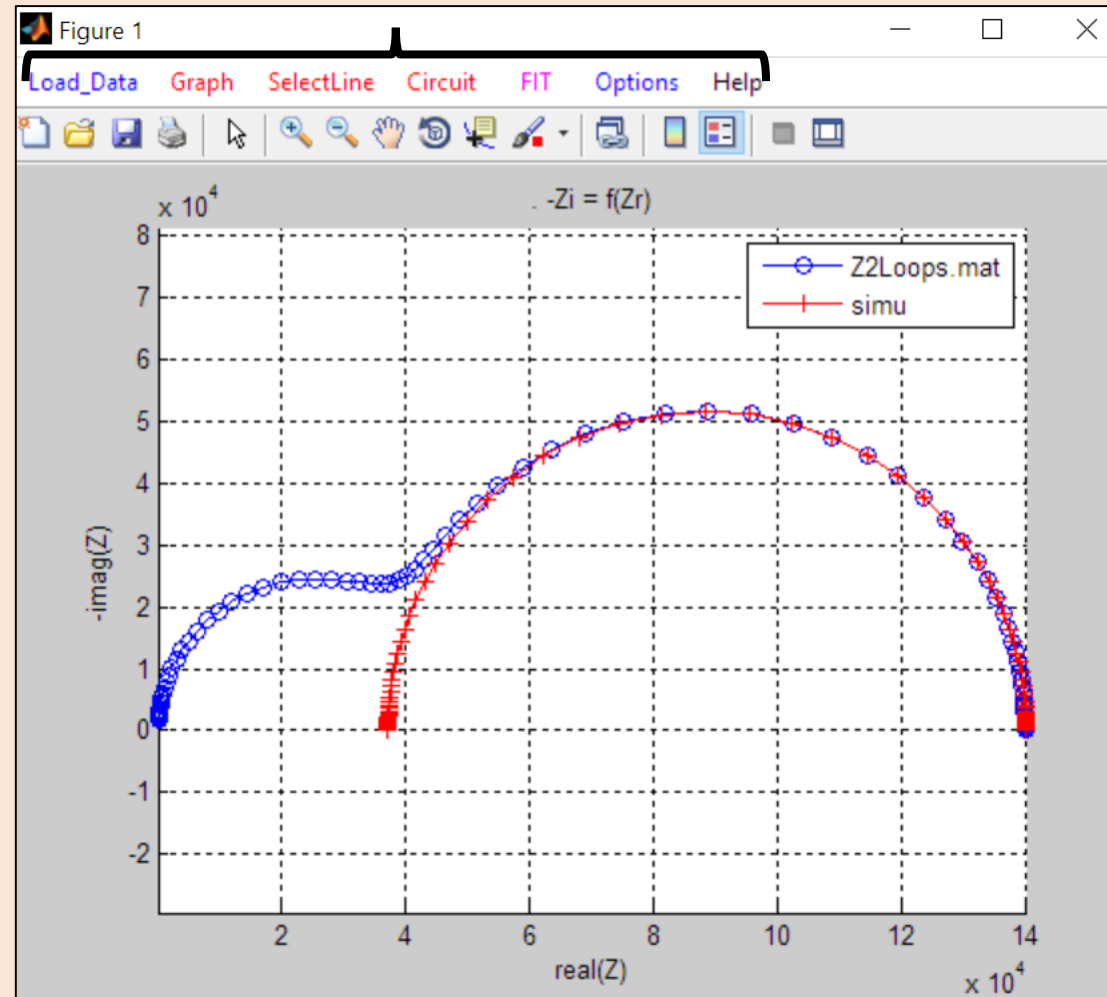


How to generate simulated Z-data

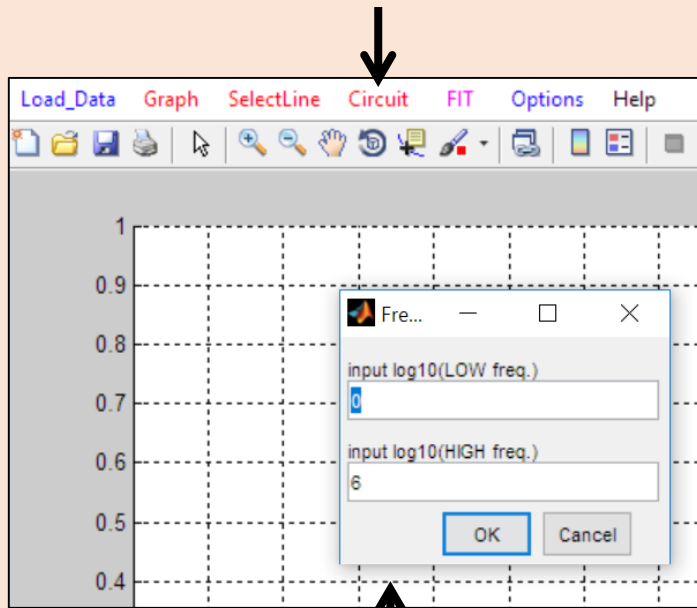


Click 'Circuit' to enter the frequency bounds.
Default : 1 Hz to 10^6 Hz...

... and to enter the Circuit String. Default string is : $s(p(R1, C1), R1)$.
's' stands for 'put in series' and 'p' for 'put in parallel'. These operators must have exactly 2 arguments. The numerals beside the element letters R (resistor) and C (capacitor) are reminders about the amount of parameters they need. L1 (inductor), E2 (CPE), G2, H2 (diffusion impedances) and even user-defined element may be used. Read the User Manual of ZfitGUI to have more details about them.

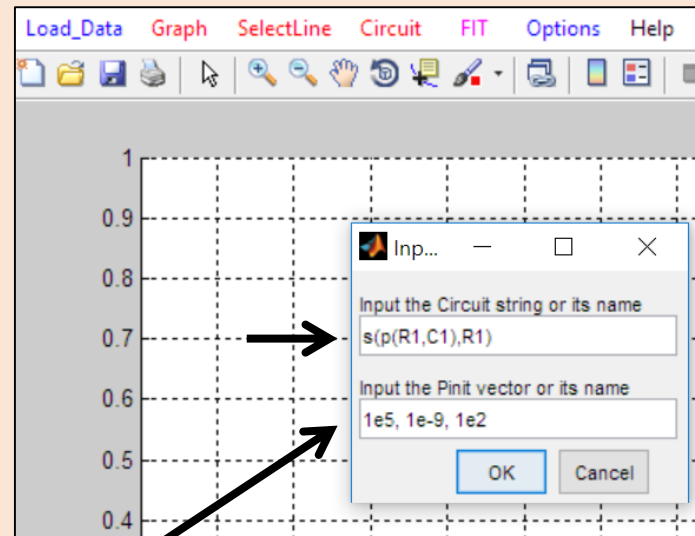


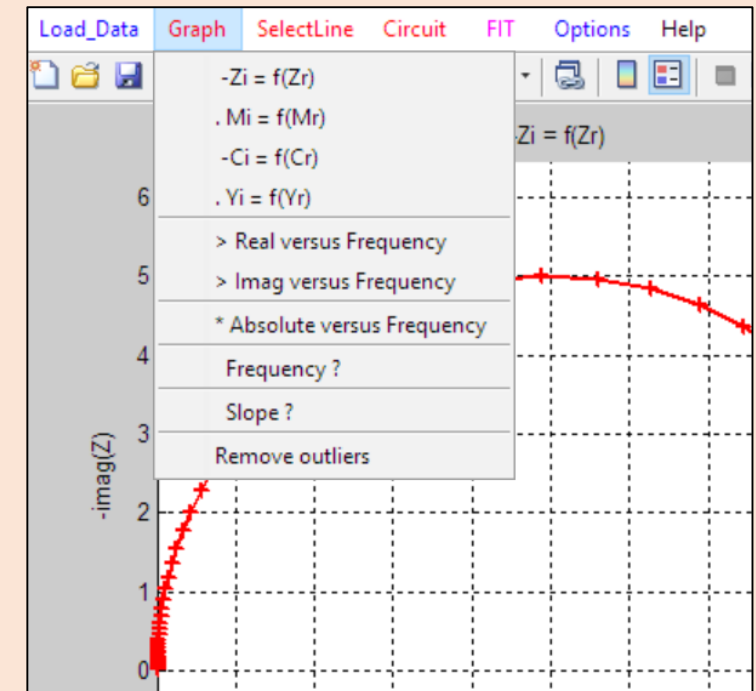
It is mandatory to enter values for the elements. Enter them as they come in the Circuit String.
Default : $5 \cdot 10^4$, 10^{-9} , $5 \cdot 10^3$



Note that 'Graph' contains sub-menus

Z2Loops – Fitting a simulated Data of a conductive system (A)

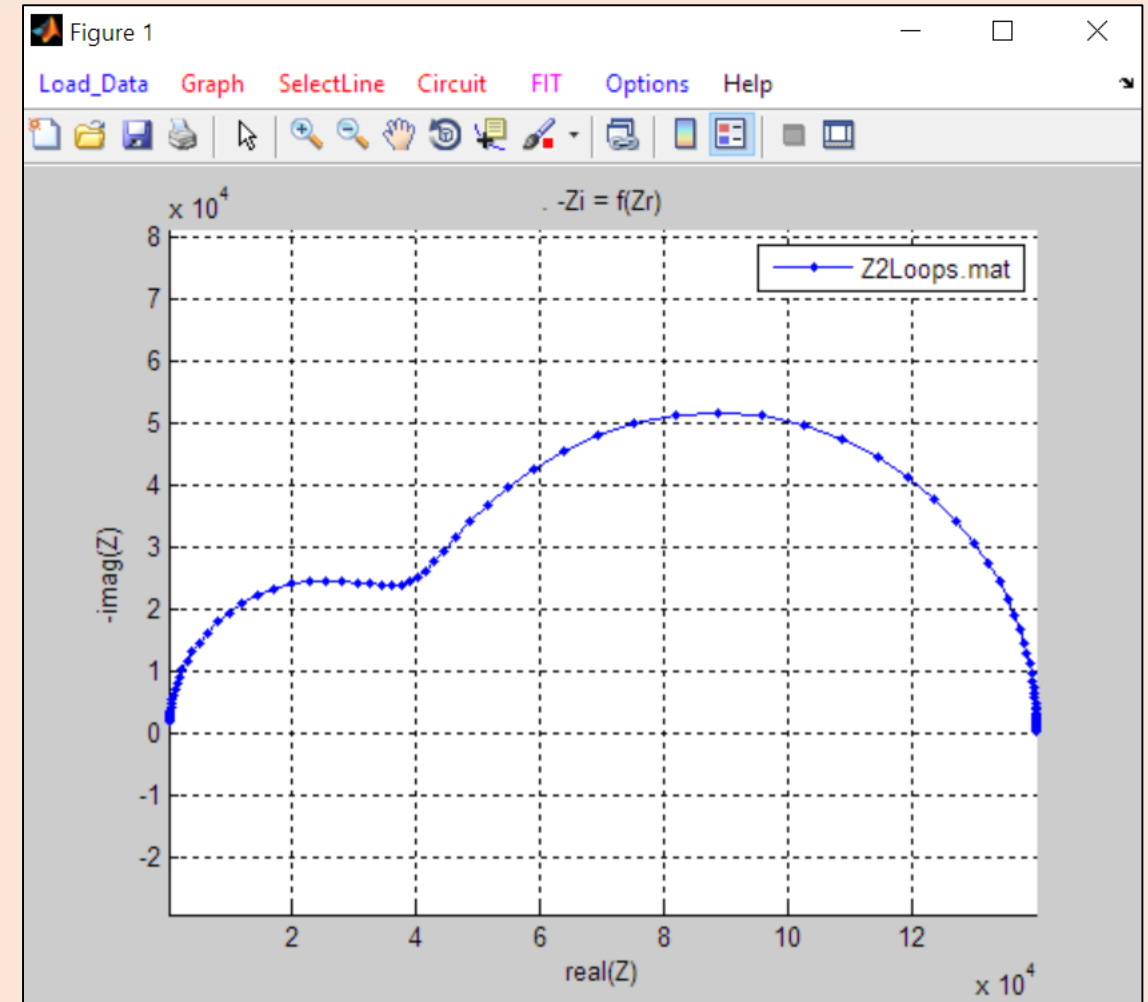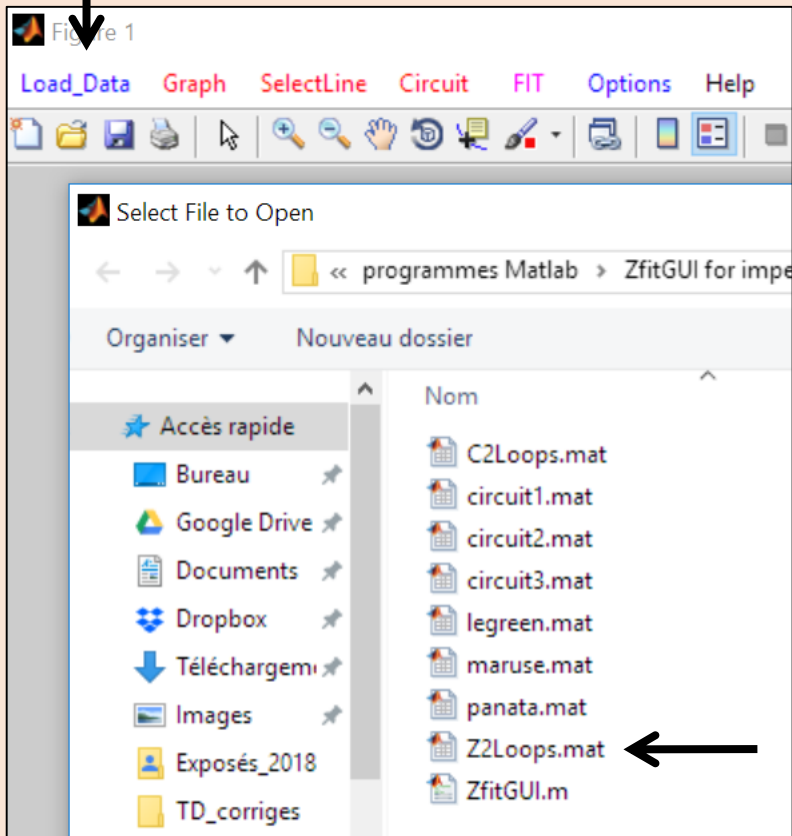
Click on the « Load Data » uimenu to load Z2Loops in ZfitGUI




Next step is to select the curve, write a Circuit string and feed it with initial values

Z2Loops – Fitting of a simulated Data of a conductive system (B)

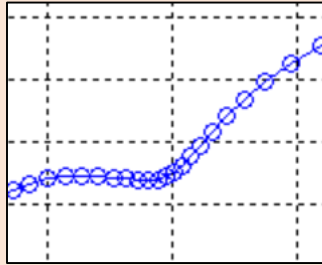
Click on
«SelectLine »
to process the
curve



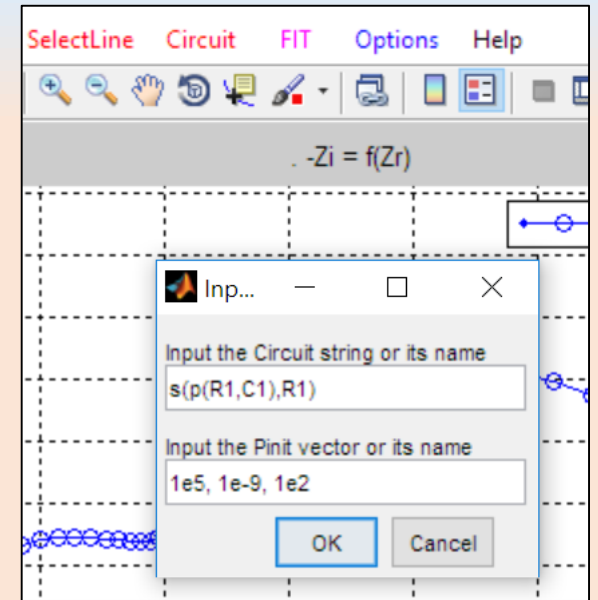Click on « Circuit » to enter the Circuit string and the Pinit. As the spectra usually show loops,
« $s(p(R1,C1),R1)$ » is a good start because $p(R1,C1)$ defines a semi-circle which can be translated along the real axis with the $s(\text{ , }R1)$ operator



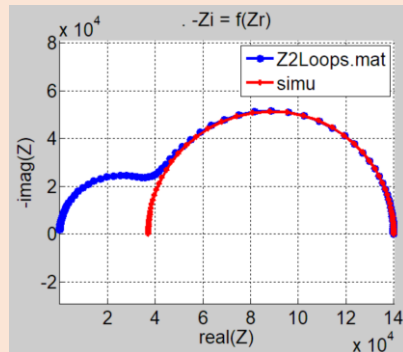... to get the results
graphically and in the
Result figure:




Click on «Fit», then twice on the
large loop to fit it and ...

Fit results for : $s(p(R1,C1),R1)$


	Value
Model	$s(p(R1,C1),R1)$
Khi2/N	1.78e-03
p(1)=	1.04e+05
p(2)=	8.73e-10
p(3)=	3.54e+04

Try to fit the whole spectrum
with $s(p(R1,C1), p(R1,C1))$


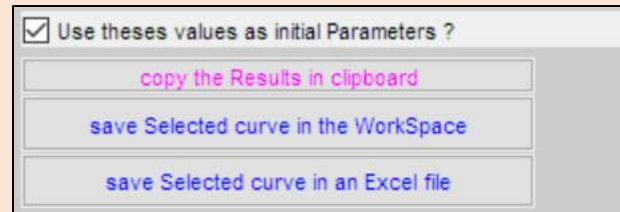
The tools in the bottom of the Result
figure are very usefull :



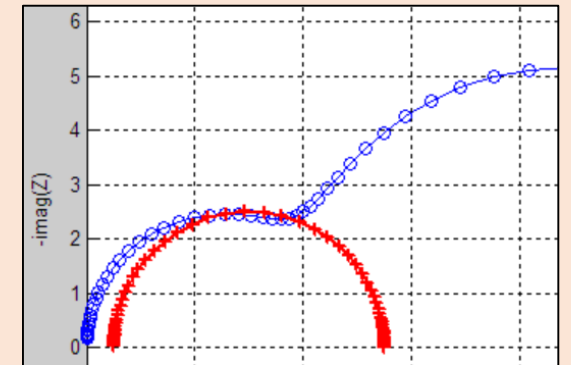Very usefull : the values in the Value
column are editable. Change them to get a
better initial parameters set.





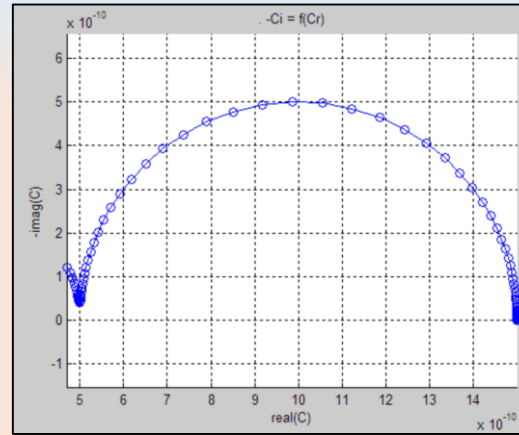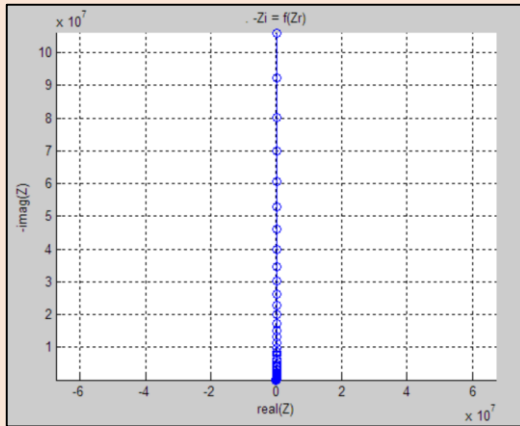C2Loops – Fitting of a simulated Data of a dielectric system




When in « C » representation, for dielectric systems, 2 successive loops correspond to 2 Debye relaxations $s(R1, C1)$ in parallel. So here, we will use the Circuit String : $p(s(R1, C1), s(R1, C1))$ and from the spectrum inspection, we shall start with capacitors $5 \cdot 10^{-10}$ F (at HF) and $15 \cdot 10^{-10}$ F (at LF).

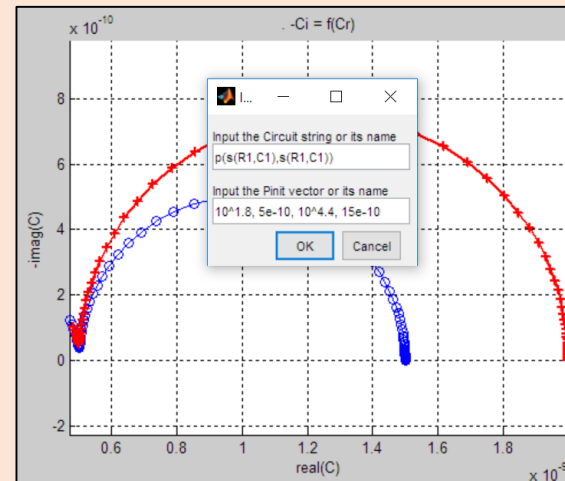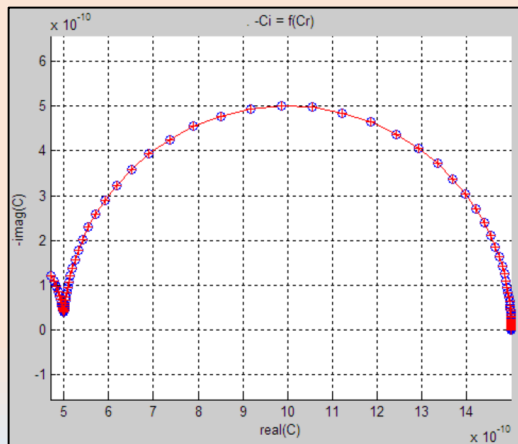Load 'C2Loops'. One obtains a Z-spectrum looking like the one of a capacitor, let's switch to : 'Graph, $-Ci=f(Cr)$ '




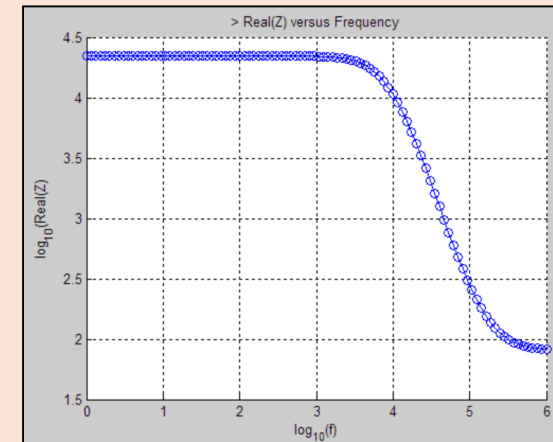The Initial parameters have little error in the C guesses but anyway, let's try « Fit »






One may examine the $Re(Z) = f(\omega)$ curve to get initial values $10^{4.4} \Omega$ (at LF) and $10^{1.8} \Omega$ (at HF) or use « Fit » and a try and error method.

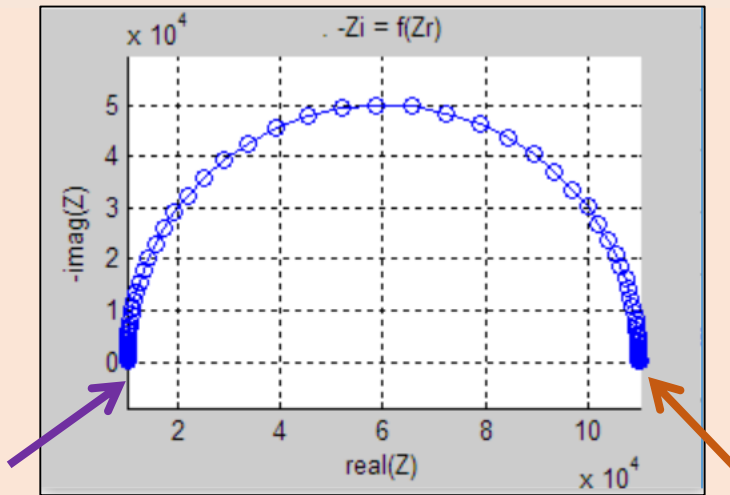Circuit1 – Pay attention to low amplitude points




Procedure :

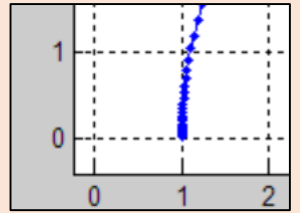Inspect the spectrum. Here, we find with the tool  and the zoom  that the semicircle is translated along the axis of the reals:





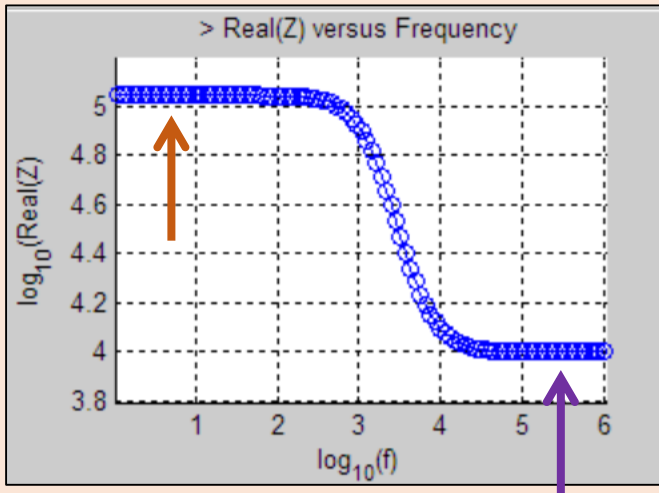
Small biases may have important consequences on the fitting success. A good strategy is to check the $\text{Re}(Z) = f(\omega)$ and the $\text{Im}(Z) = f(\omega)$ curves. One finds $\lim_{\omega \rightarrow 0} \text{Re}(Z) \approx 10^{5.05} \Omega$ and $\lim_{\omega \rightarrow \infty} \text{Re}(Z) \approx 10^4 \Omega$.



- $s(R1, p(R1, C1))$ is the right Circuit string.
- Enter the model string after clicking on the "Circuit" menu and initial (guessed) values
- Click on « FIT »
- Check the results

Very useful : with the « edit plot » tool (), you may delete any graphic object ...

Circuit2 – Simulated Data with an CPE

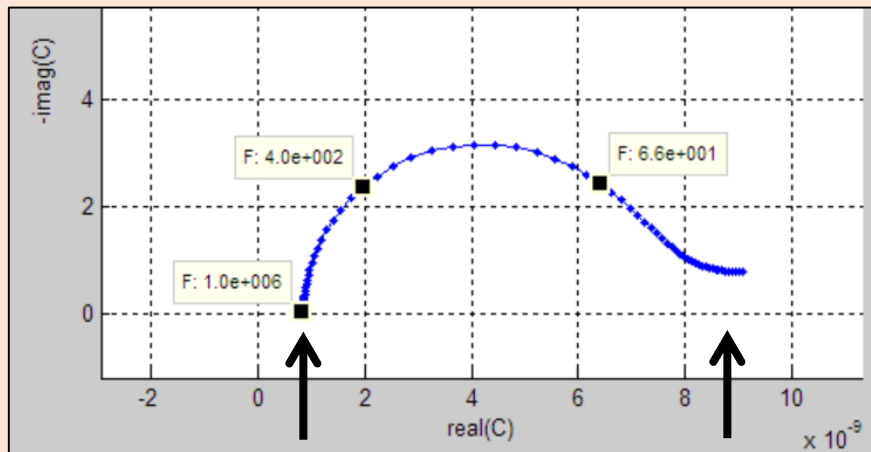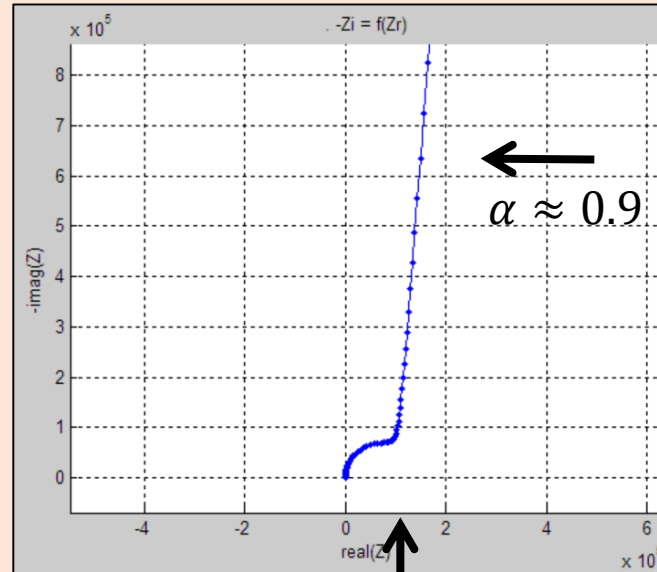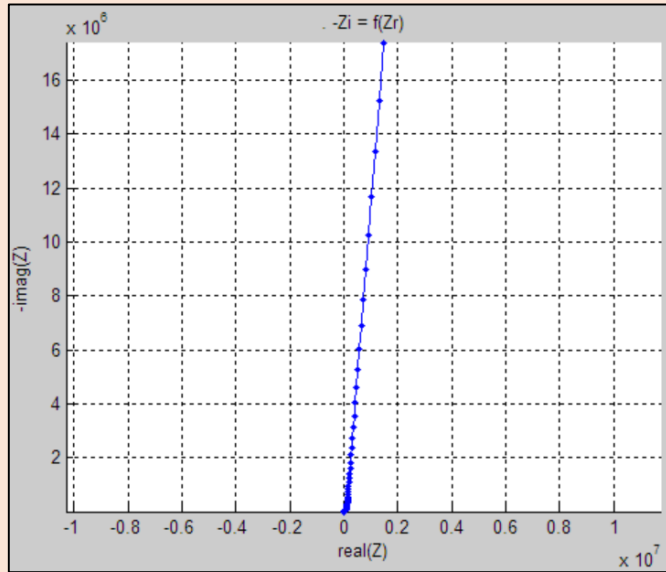

$c \approx 1e - 9$

$A \approx 9e - 9$

$r \approx 1e5$

4 Hints :





- Zoom the HF
- change graph to complex C
- use « Graph + Frequency ? »
- Remind $Z_{cpe} = \frac{1}{A(j\omega)^\alpha}$

s (p (R1, C1), E2)

Guessed Values
obtained from
inspection of the
graphs

Fit ...

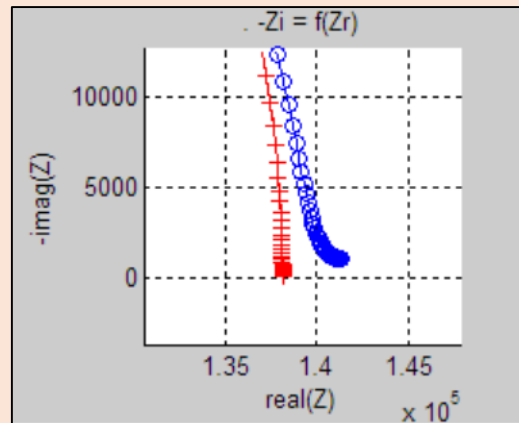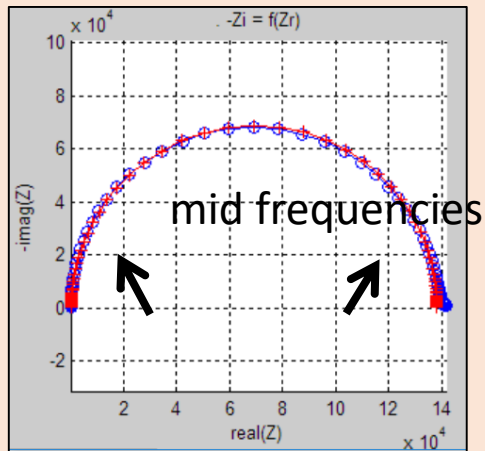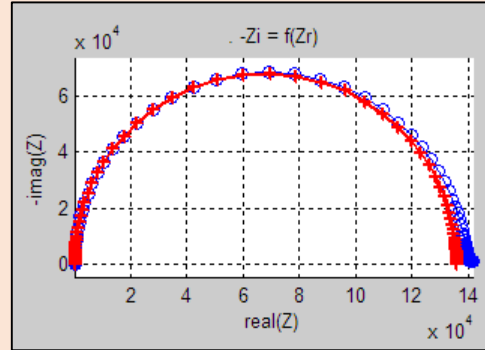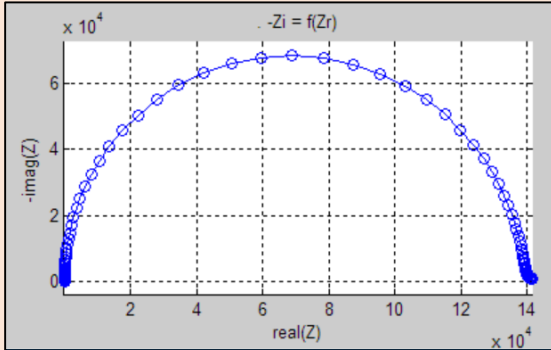
Circuit3 – Simulated Data with low frequency dispersion







Steps (example) :

- Firstly, use a simple $s(R1, p(R1, C1))$ circuit.
- Use the « Fit » tool for the HF (fig2). The RC is OK for the HF but it looks like there is another relaxation at LF $\Rightarrow s(p(R1,C1),p(R1,C1))$.
- The fit on the mid frequencies (fig3) seems enough good.
- To go further, a zoom for the LF revealed that the experimental Z came on the real axis with a different slope compared to the RC model in red (fig4) \Rightarrow try $s(p(R1,C1),p(E2,C1))$ using the initial values from fig4 (adding an exponent of 0.01 for the CPE which mimics a 'dispersive' resistor)

Fit ...

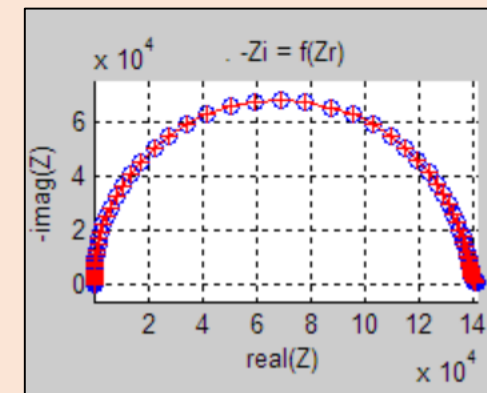


Maruse – Experimental Data

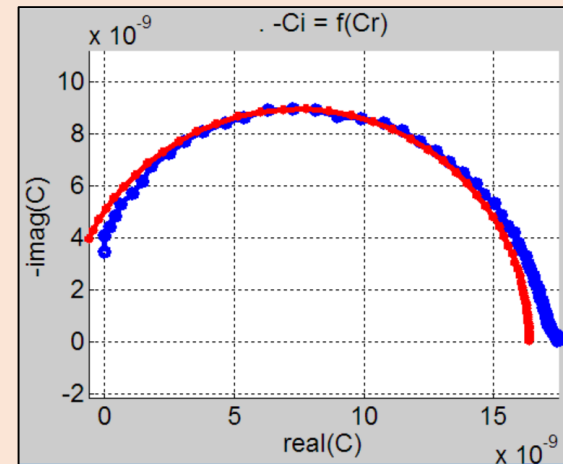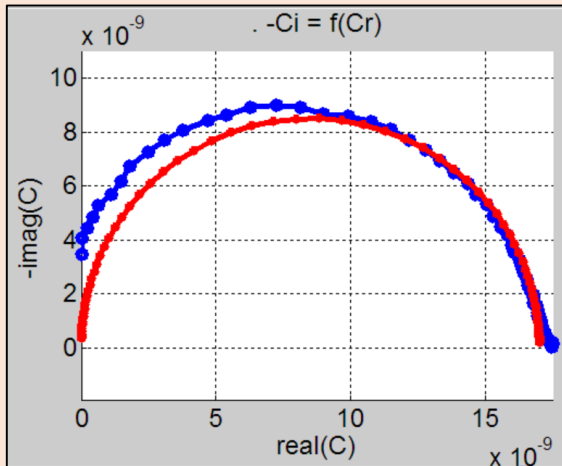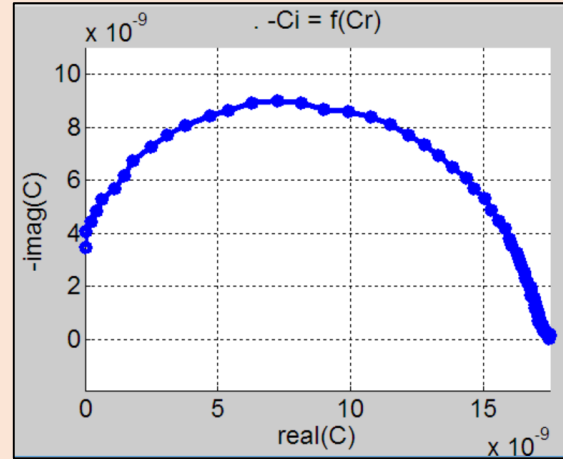
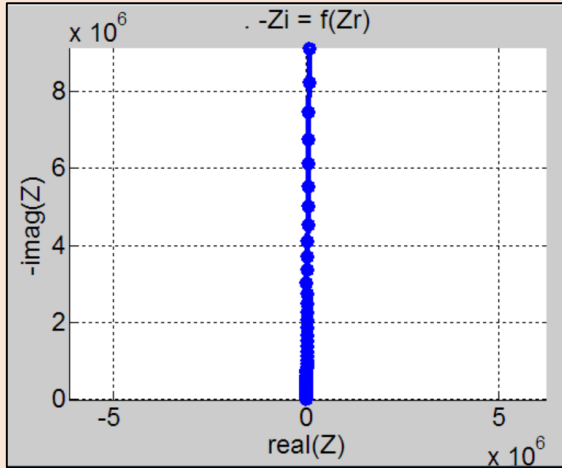


Steps (example of corrupted data) :

- The experimental HF part of the loop of fig3 (model used : $s(\text{R1}, \text{C1})$) would extrapolate to negative value !
 $\Rightarrow p(\text{C1}, s(\text{R1}, \text{C1}))$ with the first $\text{C} < 0$ initialized to $-1\text{e-}9$.
- fit the mid frequencies (fig4) or remove the outliers from the « Graph » menu (fig5) or search if CPE or diffusion impedances could improve the fitting if interested in the LF side of the system (= refine the model).

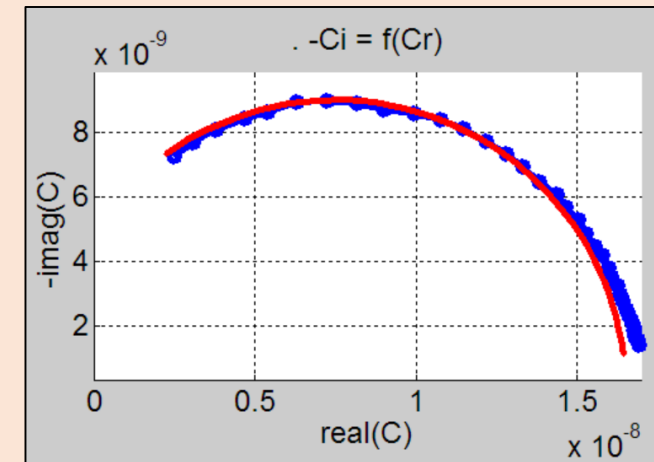

Panata – Experimental Data

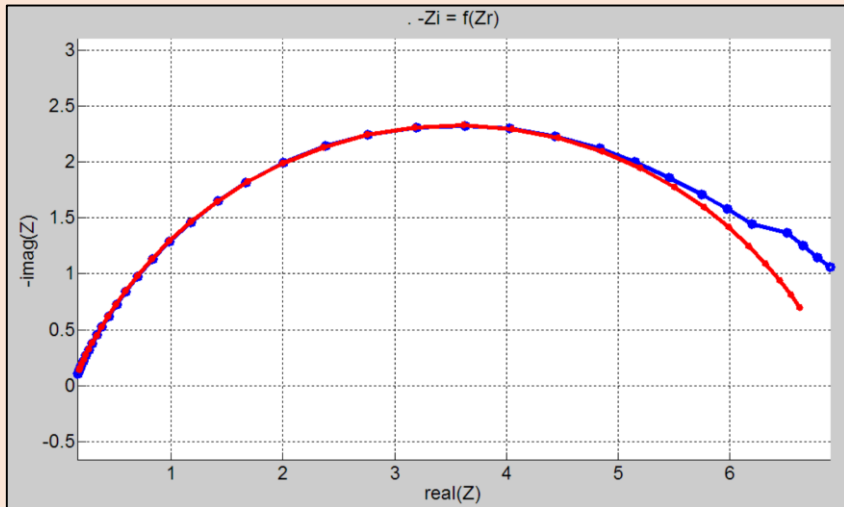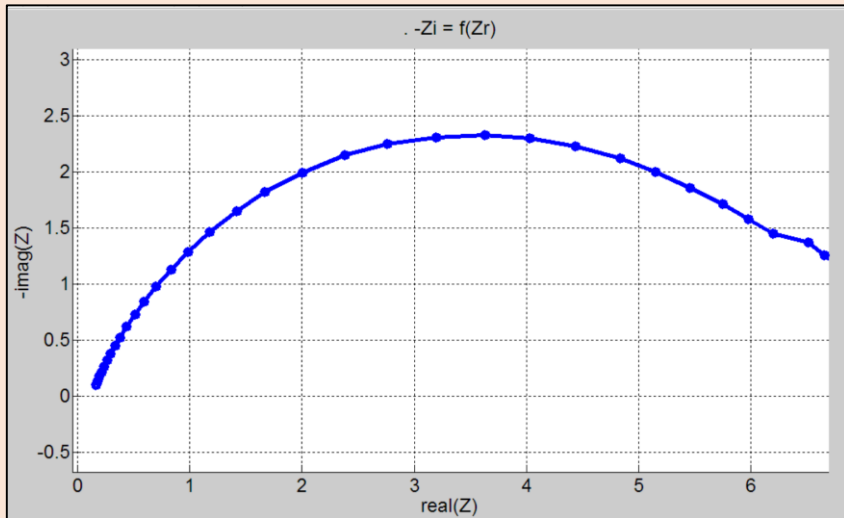

Steps (example of corrupted data) :

- Remove the HF outliers (with positive Z_i).
- Note that there is a small translation of the spectrum of $r \approx 0.1 \Omega$ (fig1).
- A semi-circle whose the center is located under the real axis can be related to a $p(R1, E2)$ circuit when in Z-representation. Adding the little resistor r , one tries $s(R1, p(R1, E2))$
- The initial values are guessed from the Z and the C representations

Fit ...

model : $s(R1, p(R1, E2))$

Khi2 of fit: $2.08e-3$

$P1 = 1.17e-1$

$P2 = 6.87e+0$



$P3 = 1.27e-3$

$P4 = 7.58e-1$

Khi2 is a measure of the distance experimental/model

Because Khi2 depends on the amount N of points taken in the fit, the normalized $\text{Khi2}/N$ is displayed in the result figure.

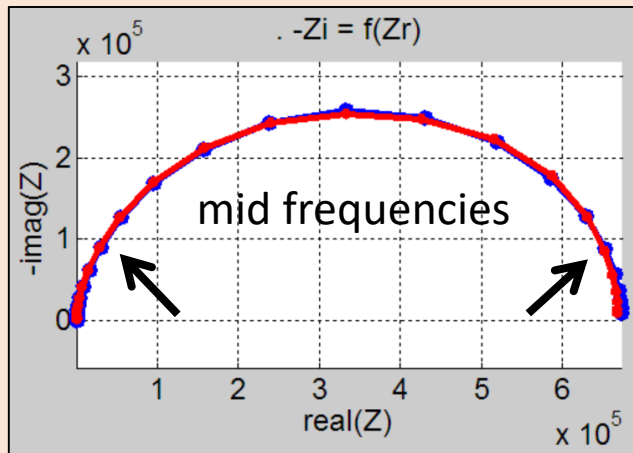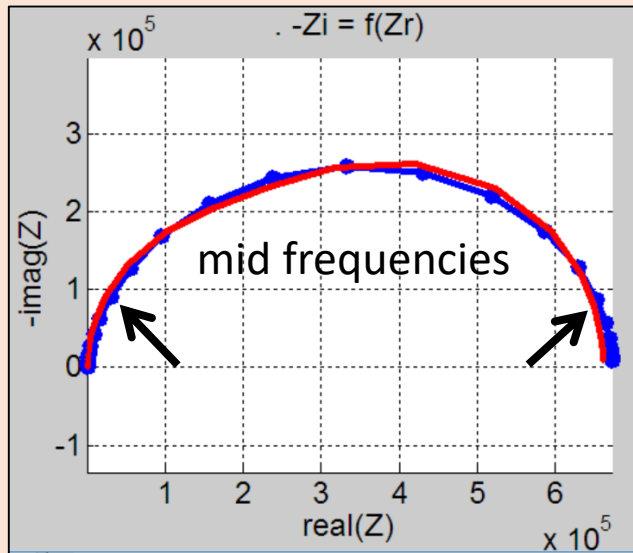Legreen – Experimental Data – a difficult case



- Using the model $s(p(R1,C1),p(R1,C1))$ and « Fit » on the mid frequencies gave fig1 with

'model : $s(p(R1,C1),p(R1,C1))$ '

'Khi2 of fit: $2.37e-2$ '

'P1 = $2.18e5$ '

'P2 = $2.19e-9$ '

'P3 = $4.43e5$ '

'P4 = $5.97e-9$ '

- Further investigations leads to use a model with a Finite Length Warburg with SHORT Circuit "G2" and a much better result altought using the same amount of parameters (4) :

'model : $p(p(R1,C1),G2)$ '


'Khi2 of fit: $9.43e-4$ '

'P1 = $7.89e5$ '

'P2 = $1.29e-9$ '



'P3 = $3.55e-8$ '

'P4 = $1.55e-1$ '

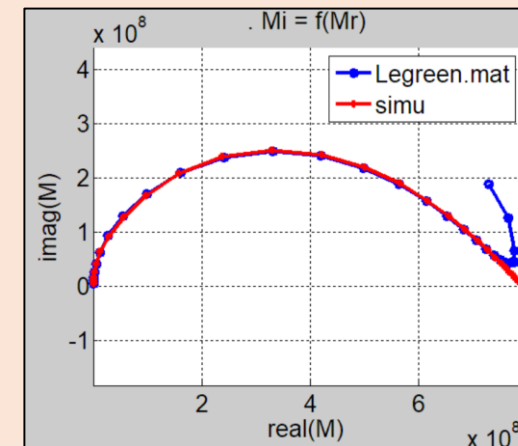


In M representation, the result is very good except at the high frequencies where there is an abnormal behavior with Mr decreasing in the experimental data. Maybe due to the apparatus ...


Ambiguity of the models

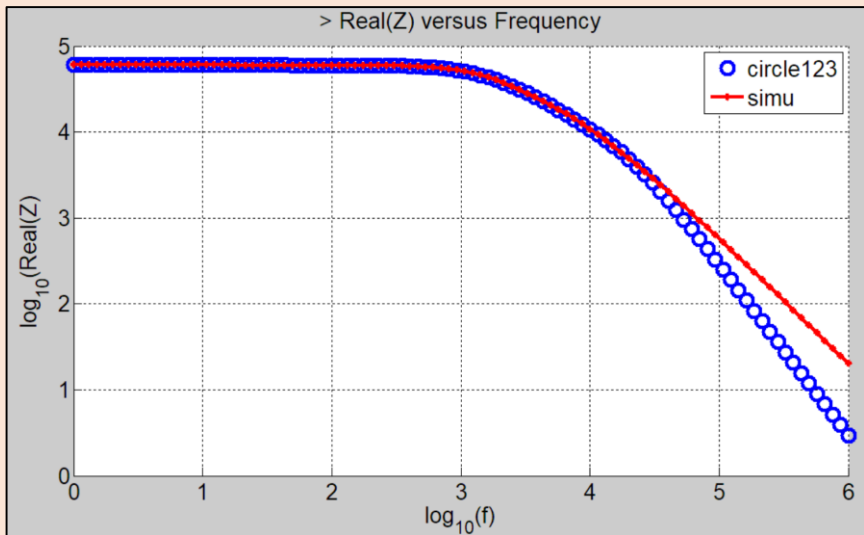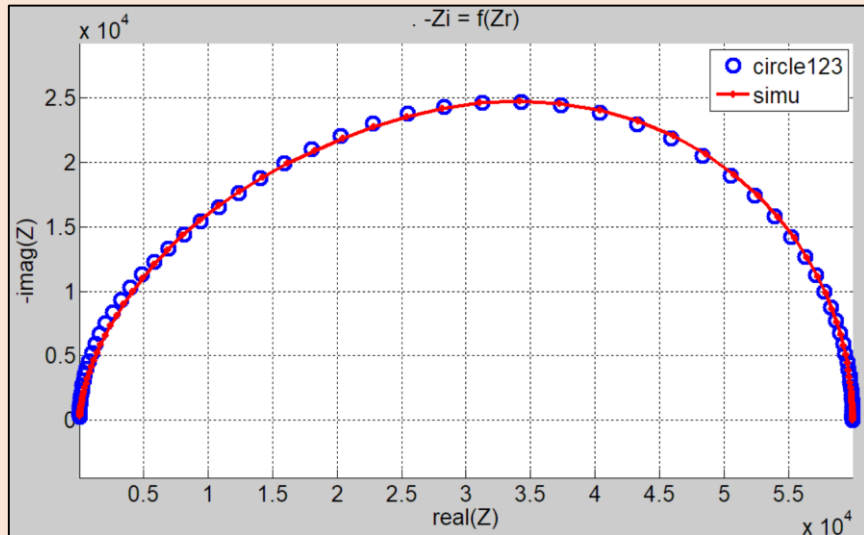

- The blue curve named « circle123 » are very similar to the experimental data processed above with a Finite Length Warburg with SHORT Circuit :
 $p(p(R1,C1),G2)$
- Try to find the parameters giving the red line which at first glance seems satisfying.
- However, watching the real Z-part gave the figure 2 where one can state a gap at the high frequencies. It is also visible when using the M-representation (figure 3).
- Read the next slide to know from where circle123 comes...

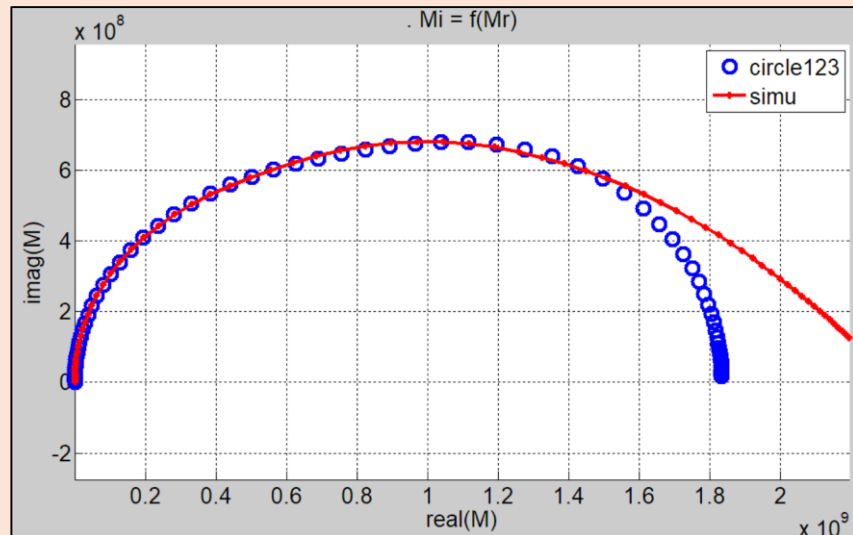

Producing simulated data

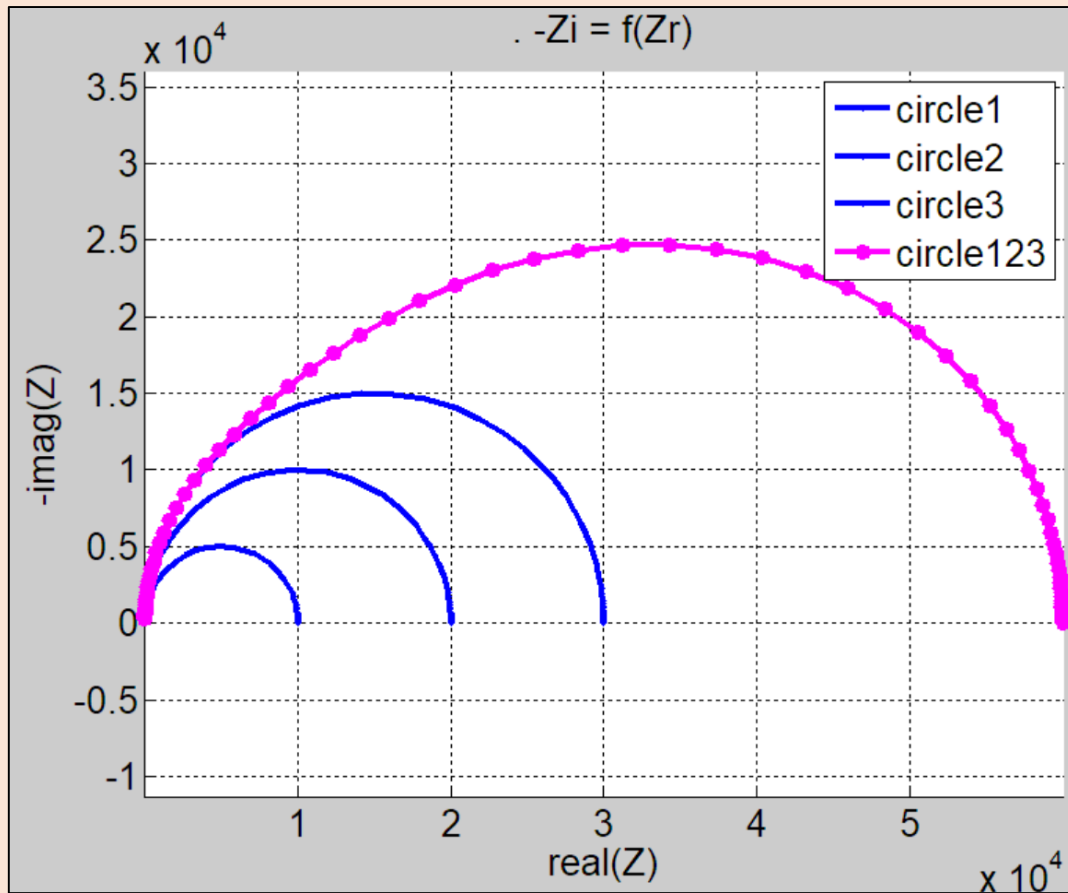

- Using the model $p(R1, C1)$ in « circuit », we produced circles 1, 2 and 3. The parameters were successively :
 $p(1) = 1e4$ then $2e4$ and $3e4$
 $p(2) = 1e-9$ then $2e-9$ and $3e-9$
- To produce the spectrum of these impedances all put in series « circle123 », the model was :
 $s(s(p(R1, C1), p(R1, C1)), p(R1, C1))$
with :
 $1e4, 1e-9, 2e4, 2e-9, 3e4, 3e-9$
- Try this model on the Legreen data ...